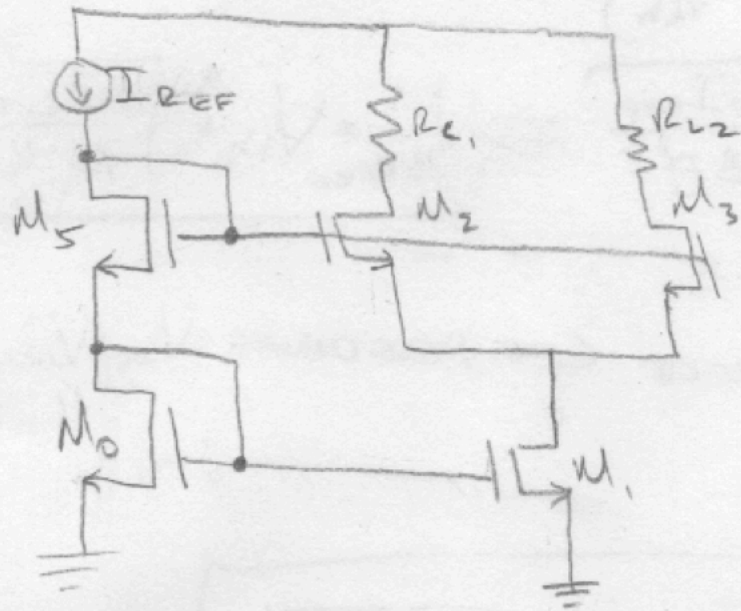


* TO GENERATE V_{BIAS2} WITHOUT AN ADDITIONAL CURRENT SOURCE I WILL USE THE TOPOLOGY BELOW:



$$I_{REF} = \frac{\beta}{2} \left(\frac{W}{L} \right)_S (V_{BIAS2} - \overbrace{2\sqrt{I_{REF}}}^{V_{OV=0}} - V_{th})^2$$

$$\left(\frac{W}{L} \right)_S = \frac{2 I_{REF}}{\beta (V_{BIAS2} - 2\sqrt{I_{REF}} + V_{th} - V_{th})^2}$$

$$\left(\frac{W}{L} \right)_S = \frac{2 I_{REF}}{\beta (2\sqrt{I_{REF}} + V_{th})^2}$$

* SENSITIVE TO PROCESS VARIATION.

* THIS CIRCUIT IS SENSITIVE TO V_{BIAS} BECAUSE IT DIRECTLY AFFECTS THE CURRENT (AND HENCE THE TRANSCONDUCTANCE AND GAIN) THROUGH M_2 & M_3 .

$$\left(\frac{W}{L} \right)_S = 10$$

channel length $L_1 = 2.5 \mu m$
 $L_2 = 0.75 \mu m$