

PART 2:  $V_{th} = 550\text{mV}$

$$I_{TAIL} = \frac{\beta}{2} \frac{W}{L} (V_{G1} - V_{th})^2$$

$$I_{TAIL} = 4\mu\text{A}$$

$$g_{m1} = g_{m2} = \sqrt{2 \left( \frac{I_{TAIL}}{2} \right) \beta \frac{W}{L}}$$

$$g_{m1} = g_{m2} = 80\mu\text{S}$$

\* WITH JUST A  $50\text{mV}$  INCREASE IN  $V_{th}$ , WE SEE THE TRANSCONDUCTANCE (AND HENCE THE GAIN) DROP BY A FACTOR OF TWO.

PART 3: (FIG. 2)

$$I_{REF} = 16\mu\text{A}$$

$$\left( \frac{W}{L} \right)_{M0} = \left( \frac{W}{L} \right)_{M1} \Rightarrow I_{TAIL} = 16\mu\text{A}$$

$$(g_{m\tau_0})_{M0} = (g_{m\tau_0})_{M1} = 10 \quad V_{D1} = 550\text{mV}$$

$$\Delta V_{DS} = -50\text{mV} = g_{m\tau_0} \Delta V_{GS} \Rightarrow \Delta V_{GS} = -0.005\text{V}$$

$$I'_{TAIL} = \frac{\beta}{2} \frac{W}{L} (V_{GS} + \Delta V_{GS} - V_{th})^2$$

$$I'_{TAIL} = 14.44\mu\text{A}$$

$$I_{REF} = \frac{\beta}{2} \frac{W}{L} (V_{GS} - V_{th})^2$$

$$V_{GS0} = 0.6\text{V} = V_{GS1}$$

PART 4:

$$V_{D1} \geq V_{OV1} \Rightarrow V_{BIAS2} - (V_{OV2} + V_{th}) - V_{OV1} = 0$$

$$V_{BIAS2} \geq 50\sqrt{I_{REF}} + V_{th}$$

$$V_{OV1} = V_{G1} - V_{th}$$

$$I_{REF} = \frac{\beta}{2} \left( \frac{W}{L} \right)_1 (V_{G1} - V_{th})^2$$

$$\sqrt{\frac{2 I_{REF}}{\beta \frac{W}{L}}} = V_{G1} - V_{th} = V_{OV1} = 25\sqrt{I_{REF}}$$

$$\frac{I_{REF}}{2} = \frac{\beta}{2} \left( \frac{W}{L} \right)_2 V_{OV}^2$$

$$V_{OV2} = \sqrt{625 I_{REF}}$$

$$V_{OV2} = 25\sqrt{I_{REF}}$$