

## PART 5: (FIG 3)

\* BECAUSE THE REFERENCE CURRENT HOLDS  $V_{BIAS2}$  FIXED, THE SOURCE VOLTAGES OF  $M_2$  &  $M_3$  CANNOT CHANGE LIKE IN PART 3. THUS THE CURRENT THROUGH  $M_1$  WILL BE MUCH MORE STABLE.

USING PARAMETERS FROM PART 4:

$$I_{REF} = \frac{\beta}{2} \left( \frac{W}{L} \right)_4 (V_{BIAS2} - \overset{V_{ov0}}{25\sqrt{I_{REF}}} - V_{th})^2$$

$$\left( \frac{W}{L} \right)_4 = \frac{2 I_{REF}}{\beta (V_{BIAS2} - 25\sqrt{I_{REF}} - V_{th})^2}$$

$$= \frac{2 I_{REF}}{\beta (25\sqrt{I_{REF}} + V_{th} - V_{th})^2}$$

$$= \frac{2 I_{REF}}{625 \beta I_{REF}}$$

$$\underline{\left( \frac{W}{L} \right)_4 = 10} \Rightarrow \boxed{\begin{aligned} W_4 &= 2.5 \mu m \\ L_4 &= 0.25 \mu m \end{aligned}}$$

## PART 6 (ADD. CREDIT)

$$V_{ov2} = 25\sqrt{2 I_{REF}}$$

$$V_{BIAS2} = 25\sqrt{2 I_{REF}} + V_{th} + 25\sqrt{I_{REF}}$$

$$V_{BIAS2} = 60.35\sqrt{I_{REF}} + V_{th}$$

$$I_{REF} = \frac{\beta}{2} \left( \frac{W}{L} \right)_4 (V_{BIAS2} - 25\sqrt{I_{REF}} - V_{th})^2$$

$$\left( \frac{W}{L} \right)_4 = \frac{2 I_{REF}}{\beta (35.35\sqrt{I_{REF}})^2}$$

$$\boxed{\left( \frac{W}{L} \right)_4 = 5}$$

$$W_4 = 1.25 \mu m$$

$$L_4 = 0.25 \mu m$$