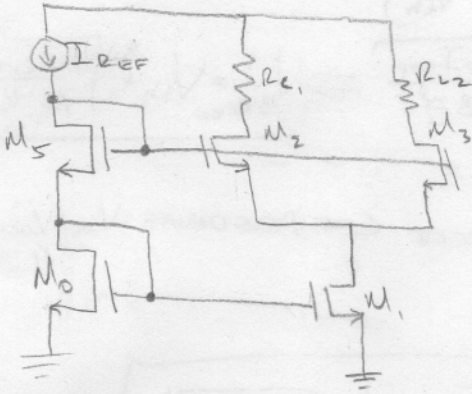


* TO GENERATE V_{BIAS2} WITHOUT AN ADDITIONAL CURRENT SOURCE I WILL USE THE TOPOLOGY BELOW:



$$I_{REF} = \frac{\beta}{2} \left(\frac{W}{L} \right)_S (V_{BIAS2} - \overbrace{25\sqrt{I_{REF}}}^{V_{OV=0}} - V_{th})^2$$

$$\left(\frac{W}{L} \right)_S = \frac{2 I_{REF}}{\beta (V_{BIAS2} - 25\sqrt{I_{REF}} + V_{th} - V_{th})^2}$$

$$\left(\frac{W}{L} \right)_S = \frac{2 I_{REF}}{\beta (25\sqrt{I_{REF}} + V_{th})^2}$$

* SENSITIVE TO PROCESS VARIATION.

* THIS CIRCUIT IS SENSITIVE TO V_{BIAS} BECAUSE IT DIRECTLY AFFECTS THE CURRENT (AND HENCE THE TRANSCONDUCTANCE AND GAIN) THROUGH M_2 & M_3 .

PART 5: (FIG 3)

* BECAUSE THE REFERENCE CURRENT HOLDS V_{BIAS2} FIXED, THE SOURCE VOLTAGES OF M_2 & M_3 CANNOT CHANGE LIKE IN PART 3. THUS THE CURRENT THROUGH M_1 WILL BE MUCH MORE STABLE.

USING PARAMETERS FROM PART 4:

$$I_{REF} = \frac{\beta}{2} \left(\frac{W}{L} \right)_4 (V_{BIAS2} - \overbrace{25\sqrt{I_{REF}}}^{V_{OV=0}} - V_{th})^2$$

$$\left(\frac{W}{L} \right)_4 = \frac{2 I_{REF}}{\beta (V_{BIAS2} - 25\sqrt{I_{REF}} - V_{th})^2}$$

$$= \frac{2 I_{REF}}{\beta (25\sqrt{I_{REF}} + V_{th} - V_{th})^2}$$

$$= \frac{2 I_{REF}}{625 \beta I_{REF}}$$

$$\left(\frac{W}{L} \right)_4 = 10 \Rightarrow \begin{cases} W_4 = 2.5 \mu m \\ L_4 = 0.25 \mu m \end{cases}$$

PART 6 (ADD. CREDIT)

$$V_{ov2} = 25\sqrt{2 I_{REF}}$$

$$V_{BIAS2} = 25\sqrt{2 I_{REF}} + V_{th} + 25\sqrt{I_{REF}}$$

$$V_{BIAS2} = 60.35\sqrt{I_{REF}} + V_{th}$$

$$I_{REF} = \frac{\beta}{2} \left(\frac{W}{L} \right)_4 (V_{BIAS2} - 25\sqrt{I_{REF}} - V_{th})^2$$

$$\left(\frac{W}{L} \right)_4 = \frac{2 I_{REF}}{\beta (35.35\sqrt{I_{REF}})^2}$$

$$\left(\frac{W}{L} \right)_4 = 5$$

$$\begin{cases} W_4 = 1.25 \mu m \\ L_4 = 0.25 \mu m \end{cases}$$