

Problem Set 3

MILES SHERMAN

$$\beta = 320 \frac{\mu A}{V^2}$$

$$I_{DS} = \frac{\beta}{2} \frac{W}{L} (V_{GS} - V_{th})^2, V_{th} = 500mV$$

PART 1 (FIG 1)

$$1.8V - (150k\Omega)I_L = 0$$

$$I_L = 12\mu A$$

$$1.8 - (12\mu A)(100k\Omega) = V_{G1}$$

$$\underline{V_{G1} = 0.6V}$$

$$g_{m1} = g_{m2} = \sqrt{2 \left(\frac{I_{TAIL}}{2} \right) \beta \frac{W}{L}}$$


$$\boxed{g_{m1} = g_{m2} = 0.16mS}$$

FOR MAX GAIN & STILL IN SATURATION:

$$1.8 - (R_{L1}) \left(\frac{I_{TAIL}}{2} \right) - V_{OV_{2,3}} - V_{OV1} = 0$$

$$- R_{L1} = (V_{OV_{2,3}} + V_{OV1} - 1.8) / (I_{TAIL}/2)$$

$$\boxed{R_{L1} = R_{L2} = 200k\Omega}$$

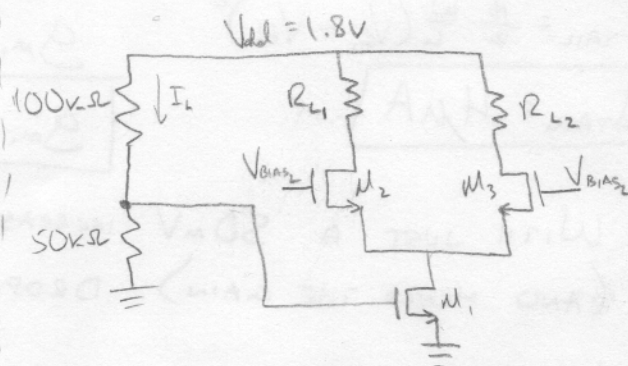

$$I_{DS1} = I_{TAIL} = \frac{\beta}{2} \frac{W}{L} (V_{G1} - V_{th})^2$$

$$\boxed{I_{TAIL} = 16\mu A}$$

$$\frac{I_{TAIL}}{2} = \frac{\beta}{2} \frac{W}{L} (V_{OV_{2,3}})^2 \quad \text{FOR } M_2 \text{ \& } M_3$$

$$\underline{V_{OV_{2,3}} = 0.1V}$$

$$\underline{V_{OV1} = 0.1V}$$

*THE GAIN OF THE DIFF-AMP INCREASES WITH R_{L1} & R_{L2} (ASSUMING THEIR VALUES ARE EQUAL. HOWEVER, IF THE VOLTAGE DROP ACROSS THE RESISTORS IS TOO HIGH, M_2 WILL FALL OUT OF SATURATION.